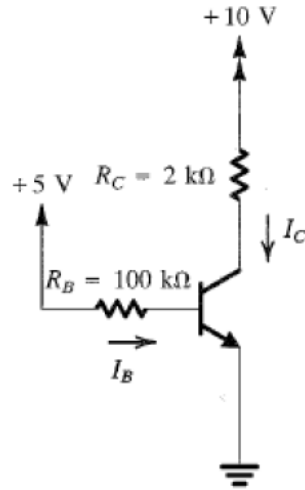


Yanda gösterilen devrede transistörde  $\beta=100$  ve  $V_{BE}=0.7$  V dir. Transistör üzerindeki akım ve gerilimleri bulunuz.



### Çözüm


$$I_B = \frac{+5 - V_{BE}}{R_B} \approx \frac{5 - 0.7}{100} = 0.043 \text{ mA}$$

$$I_C = \beta I_B = 100 \times 0.043 = 4.3 \text{ mA}$$

$$V_C = +10 - I_C R_C = 10 - 4.3 \times 2 = +1.4 \text{ V}$$

$$V_B = V_{BE} \approx +0.7 \text{ V}$$

$$I_E = (\beta + 1) I_B = 101 \times 0.043 \approx 4.3 \text{ mA}$$

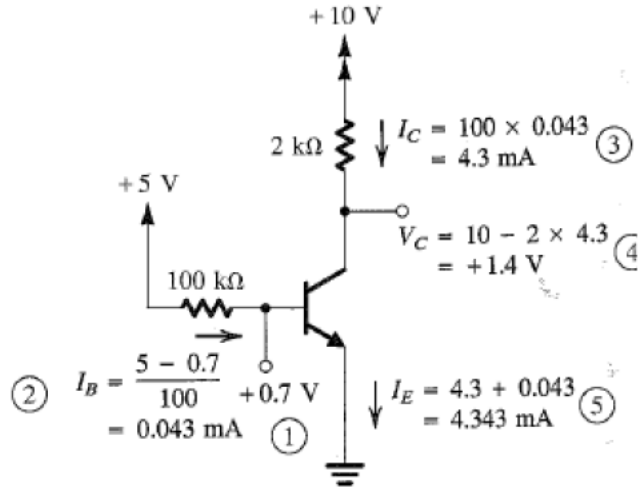

**Example 1:** Compute the parameters of this circuit ( $\beta = 100$ ).

Following the procedure above:

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE}$$

$$\text{CE-KVL: } 12 = 10^3 i_C + v_{CE},$$

Assume BJT is in cut-off. Set  $i_B = 0$  in BE-KVL:

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} \rightarrow v_{BE} = 4 > v_\gamma = 0.7 \text{ V}$$

So BJT is not in cut off and BJT is ON. Set  $v_{BE} = 0.7 \text{ V}$  and use BE-KVL to find  $i_B$ .


$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} \rightarrow i_B = \frac{4 - 0.7}{40,000} = 82.5 \mu\text{A}$$

Assume BJT is in active linear, Find  $i_C = \beta i_B$  and use CE-KVL to find  $v_{CE}$ :

$$i_C = \beta i_B = 100 i_B = 8.25 \text{ mA}$$

$$\text{CE-KVL: } 12 = 1,000 i_C + v_{CE}, \rightarrow v_{CE} = 12 - 8.25 = 3.75 \text{ V}$$

As  $v_{CE} = 3.75 > v_\gamma$ , the BJT is indeed in active-linear and we have:  $v_{BE} = 0.7 \text{ V}$ ,  $i_B = 82.5 \mu\text{A}$ ,  $i_E \approx i_C = 8.25 \text{ mA}$ , and  $v_{CE} = 3.75 \text{ V}$ .

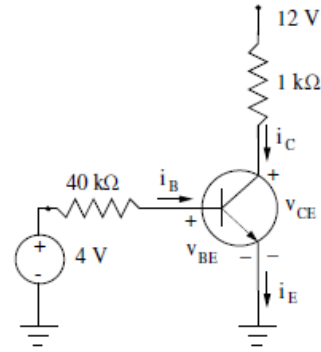

**Example 2:** Compute the parameters of this circuit ( $\beta = 100$ ).

Following the procedure above:


$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} + 10^3 i_E$$

$$\text{CE-KVL: } 12 = 1,000 i_C + v_{CE} + 1,000 i_E$$

Assume BJT is in cut-off.

Set  $i_B = 0$  and  $i_E = i_C = 0$  in BE-KVL:
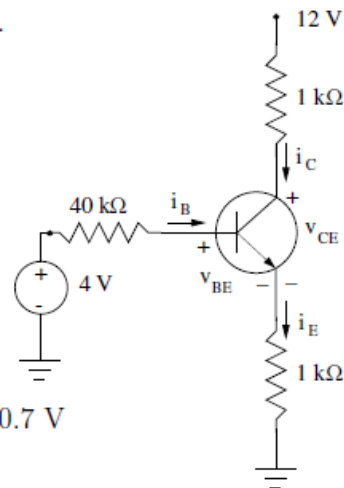
$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} + 10^3 i_E \rightarrow v_{BE} = 4 > 0.7 \text{ V}$$



So BJT is not in cut off and  $v_{BE} = 0.7 \text{ V}$  and  $i_B > 0$ . Here, we cannot find  $i_B$  right away from BE-KVL as it also contains  $i_E$ .

Assume BJT is in active linear,  $i_E \approx i_C = \beta i_B$ :

$$\begin{aligned}\text{BE-KVL: } \quad 4 &= 40 \times 10^3 i_B + v_{BE} + 10^3 \beta i_B \\ 4 - 0.7 &= (40 \times 10^3 + 10^3 \times 10^2) i_B\end{aligned}$$

$$i_B = 24 \mu\text{A} \quad \rightarrow \quad i_E \approx i_C = \beta i_B = 2.4 \text{ mA}$$

$$\text{CE-KVL: } \quad 12 = 1,000 i_C + v_{CE} + 1,000 i_E, \quad \rightarrow \quad v_{CE} = 12 - 4.8 = 7.2 \text{ V}$$

As  $v_{CE} = 7.2 > v_\gamma$ , the BJT is indeed in active-linear and we have:  $v_{BE} = 0.7 \text{ V}$ ,  $i_B = 24 \mu\text{A}$ ,  $i_E \approx i_C = 2.4 \text{ mA}$ , and  $v_{CE} = 7.2 \text{ V}$ .